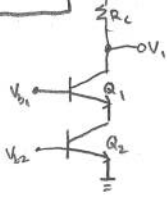


## Homework 11

9.2  $V_{CC} = 2.5V$ (a) bias current:  $0.5mA$ 

$$V_T \ln\left(\frac{I_C}{I_S}\right) = V_{BE}$$

$$V_{b2} = V_{BE2} = V_T \ln\left(\frac{I_{B2}/\alpha^2}{I_S}\right) = (0.026) \ln\left(\frac{0.00051}{6E-17}\right) = \boxed{0.774V}$$

$$V_{b1} = V_{CE2} + V_{BE1} = V_{b2} - 0.3 + V_{BE1} = 0.774 - 0.3 + (0.026) \ln\left(\frac{0.0005}{6E-17}\right) = \boxed{1.248V}$$


(b)  $V_{b2} > 0.3$ 

$$V_1 = V_{b1} - 0.3 = 0.948$$

$$V_{CC} - I_B R_C = V_1$$

$$2.5 - 0.0005 R_C = 0.948 \quad R_C = \boxed{3104\Omega}$$

9.5

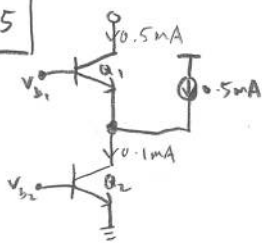 $\beta = 100$   $V_A = 5V$   $I_{C1} = 0.0005$   $I_{C2} = 0.0001$ 

$$R_{out} = g_{m1} r_{o1} (r_{o2} \parallel r_{\pi 1})$$

$$g_{m1} = \frac{I_{C1}}{V_T} \quad r_{o1} = \frac{V_A}{I_{C1}}$$


$$r_{o2} = \frac{V_A}{I_{C2}} \quad r_{\pi 1} = \frac{\beta V_T}{I_{C1}}$$

$$g_{m1} = 0.019231 \quad r_{o1} = 1E4 \quad r_{o2} = 5E4 \quad r_{\pi 1} = 5200$$

$$R_{out} = (0.019231)(1E4) \frac{(5E4)(5200)}{5E4 + 5200} = \boxed{966k\Omega}$$

9.12

$$R_{out} \geq 50k\Omega; I_B = 0.5mA; \mu_n \epsilon_{ox} = 100E-6; \frac{W}{L} = \frac{20}{0.18}$$

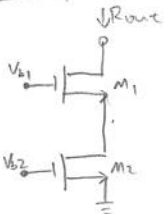maximum tolerable  $\lambda_{1,2}$ 


$$R_{out} \approx g_{m1} r_{o1} r_{o2} \geq 50k \quad I_B = I_{D1} = I_{D2} = 0.5mA$$

$$g_{m1} = \sqrt{2\mu_n \epsilon_{ox} \frac{W}{L} I_D} = 0.003333$$

$$r_{o2} = r_{o1} = \frac{1}{I_D \lambda} \quad \left(\frac{1}{(5E-4)\lambda}\right) \left(\frac{1}{(5E-4)\lambda}\right) (0.003333) \geq 50k$$

$$\boxed{\lambda \leq 0.516V^{-1}}$$

9.14

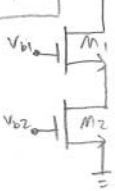

$$\left(\frac{W}{L}\right)_1 = \frac{30}{0.18} \quad \left(\frac{W}{L}\right)_2 = \frac{20}{0.18} \quad I_B = 0.5mA \quad \mu_n \epsilon_{ox} = 100E-6 \quad V_{TH} = 0.4$$

$$(2) I_{D2} = 0.5mA \quad V_{b2} = V_{GS} \quad I_{D2} = \frac{1}{2} \mu_n \epsilon_{ox} \frac{W}{L}_2 (V_{GS} - V_{TH})^2 \Rightarrow 5E-4 = \frac{1}{2} (100E-6) \left(\frac{20}{0.18}\right) (V_{b2} - 0.4)^2$$

$$\boxed{V_{b2} = 0.7V}$$

$$V_{DS2} = V_{GS2} - V_{TH} = 0.3V$$

$$V_{b1} = V_{GS1} + V_{DS2}$$

$$I_{D1} = \frac{1}{2} \mu_n \epsilon_{ox} \frac{W}{L}_1 (V_{GS1} - V_{TH})^2 \Rightarrow 5E-4 = \frac{1}{2} (100E-6) \left(\frac{30}{0.18}\right) (V_{GS1} - 0.3)^2 \quad V_{GS1} = 0.645$$

$$\boxed{V_{b1} = 0.945V}$$

(b)


$$R_{out} = g_{m1} r_{o1} r_{o2}$$

$$g_{m1} = \sqrt{2\mu_n \epsilon_{ox} \frac{W}{L}_1 I_{D1}} = \sqrt{2(100E-6) \left(\frac{30}{0.18}\right) (5E-4)} = 0.004082$$

$$r_{o1} = \frac{1}{I_{D1} \lambda} = \frac{1}{(5E-4)(0.1)} = 2E4 = r_{o2}$$

$$\boxed{R_{out} = 1.63M\Omega}$$

## Homework 11

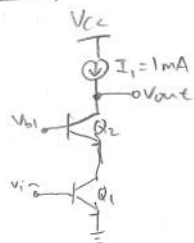9.21  $A_V = 500$   $\beta_1 = \beta_2 = 100$   $I_1 = 1 \text{ mA}$  Find minimum  $V_{A1} = V_{A2}$ 

$$A_V = -g_{m1} r_{o1} g_{m2} (r_{o1} \parallel r_{o2})$$

$$g_{m1} = \frac{I_{C1}}{V_T} = 0.038462$$

$$r_{o1} = \frac{V_A}{I_{C1}} \quad r_{o2} = \frac{\beta}{g_{m2}} = \frac{\beta V_T}{I_{C2}} = 2600$$

$$500 = - (0.038462)^2 \frac{V_A}{0.001} \frac{\frac{V_A}{I_{C1}} \cdot 2600}{\frac{V_A}{I_{C1}} + 2600}$$

$$V_A = 0.65 \text{ V}^{-1}$$

$$9.37 \quad I_1 = \frac{1}{2} \mu_{ox} \frac{W}{L} \left( \frac{R_2}{R_1 + R_2} V_{DD} - V_{TH} \right)^2$$

$$\frac{dI_1}{dV_{TH}} = -\mu_{ox} \frac{W}{L} \left( \frac{R_2}{R_1 + R_2} V_{DD} - V_{TH} \right)$$

The issue is more serious at lower voltages, because as  $V_{DD}$  goes down,  $V_{TH}$  will be relatively larger. This would mean that  $V_{TH}$  would control more of the sensitivity.

$$9.46 \quad (a) \quad I_{copy} = \frac{n I_{REF}}{1 + \frac{1}{\beta}(n+1)} = \frac{5 I_{REF}}{1 + \frac{6}{\beta}} = \frac{\beta}{\beta + 6} 5 I_{REF}$$

$$(b) \quad I_{copy} = \frac{\frac{1}{5} I_{REF}}{1 + \frac{1}{\beta}(\frac{6}{5})} = \frac{I_{REF}}{5(1 + \frac{6}{5\beta})} = \frac{I_{REF}}{5 + \frac{6}{\beta}} = \frac{\beta}{5\beta + 6} I_{REF}$$

$$(c) \quad I_{copy} = \frac{3}{2} I_{C,REF} \quad I_2 = \frac{5}{2} I_{C,REF} \quad I_{REF} = I_{C,REF} + I_{B,REF} + I_{B1} + I_{B2}$$

$$= I_{C,REF} + \frac{I_{C,REF}}{\beta} + \frac{I_{copy}}{\beta} + \frac{I_2}{\beta} = I_{C,REF} + \frac{I_{C,REF}}{\beta} + \frac{3 I_{C,REF}}{2\beta} + \frac{5 I_{C,REF}}{2\beta} = I_{C,REF} \left( 1 + \frac{1}{\beta} + \frac{3}{2\beta} + \frac{5}{2\beta} \right)$$

$$= \frac{2}{3} I_{copy} \left( \frac{5\beta}{\beta} \right) \quad \boxed{I_{copy} = \frac{3}{2} I_{REF} \left( \frac{\beta}{5\beta} \right)}$$