
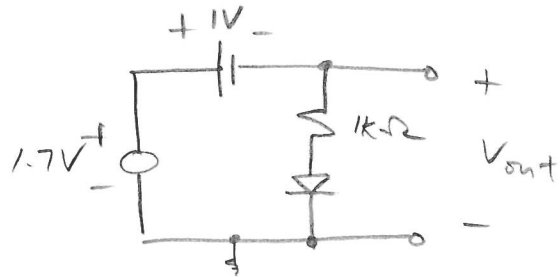


1. Find V_{out} . $V_{D,on} = 0.8V$

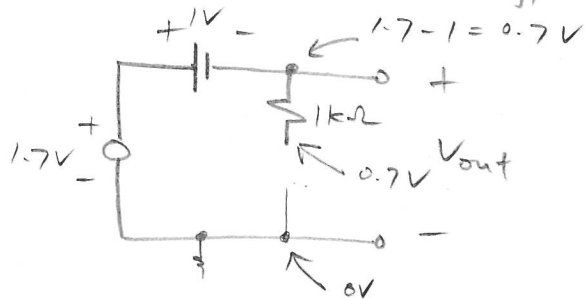


Assume the diode is off




The volt. across the diode $< V_{D,on} \rightarrow$ assumption correct.
 $\Rightarrow V_{out} = 0.7V$

2. Find V_{out} . $V_{D,on} = 0.8V$

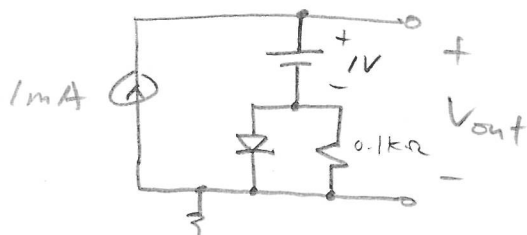


Assume the diode is off

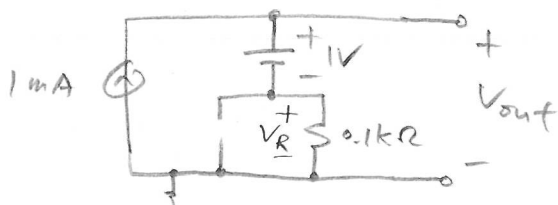

$V_R = 1mA \times 0.1k\Omega = 0.1V < V_{D,on} \rightarrow$ assumption correct
 $V_{out} = 0.1 + 1 = 1.1V$

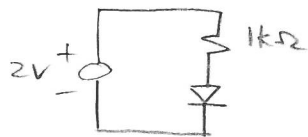
3. Assume the volt. across the diode when it is on is 0.8V. Find I_S .



$$I_D = I_S e^{V_D/V_T} = \frac{2 - 0.8}{1k} = 1.2 \text{ mA}$$

$$I_S = \frac{1.2 \text{ mA}}{e^{0.8/26 \text{ m}}} = 5.2 \times 10^{-17} \text{ A}$$

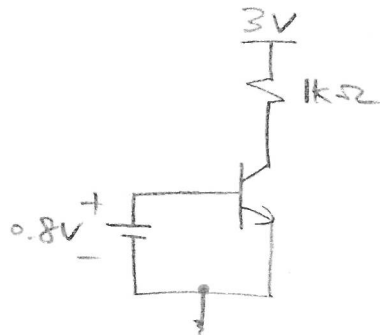4. Find I_S such that the transistor is at the edge of sat.



At the edge when $V_{CE} = V_{BE} = 0.8 \text{ V}$


$$V_{CE} = 3 \text{ V} - I_C \times 1k$$

$$I_C = I_S e^{V_{BE}/V_T}$$

$$0.8 = 3 - I_S e^{V_{BE}/V_T} \times 1k$$

$$I_S = \frac{3 - 0.8}{e^{0.8/26 \text{ m}} \times 1k} = 9.54 \times 10^{-17} \text{ A}$$

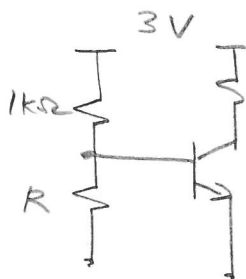5. Find R . $I_S = 10^{-17}$, $I_C = 1 \text{ mA}$.




$$V_{BE} = V_T \ln \frac{I_C}{I_S} = 0.838 \text{ V}$$

$$V_{BE} = 3 \times \frac{R}{R + 1k} = 0.838$$


$$3R = 0.838R + 838$$

$$R = 388 \Omega$$

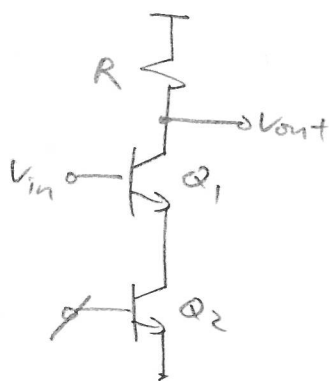6. Find gain. $V_{A_1} = \infty$, $V_{A_2} \neq \infty$.




S.S.

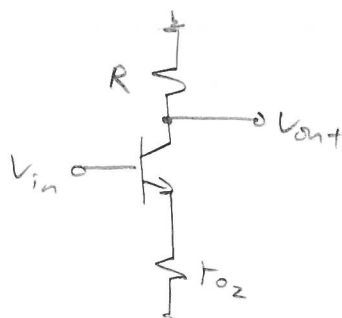


$$\frac{V_{out}}{V_{in}} = \frac{-g_m R}{1 + g_m r_{O2}}$$

7. Find R_{out} . $V_A = \infty$

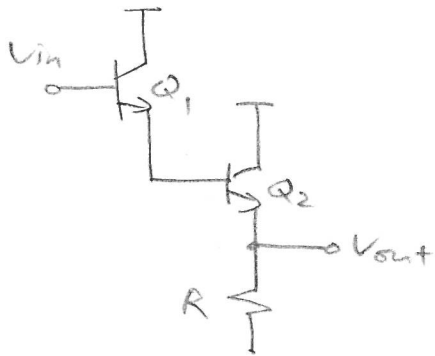


S.S.

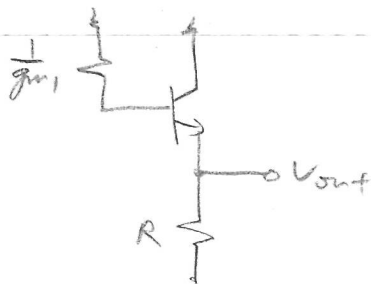

From table:

$$R_{out} = \left(\frac{1}{g_{m2}} + \frac{1/g_{m1}}{\beta_2} \right) \parallel R$$

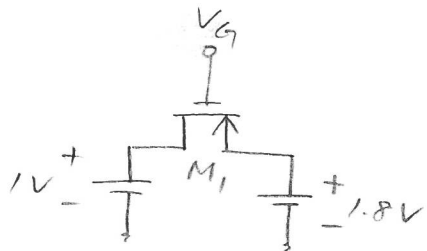8. What V_G is needed to bias M_1 at the edge of Sat. ? $V_{th} = 0.5V$



M_1 is PMOS

At edge when $V_{SD} = V_{SG} - V_{th}$


$$V_{SD} = V_S - V_G - V_{th}$$

$$V_G = V_S - V_{th} - V_{SD}$$

$$= 1.8 - 0.5 - (1.8 - 1)$$

$$= 0.5V$$

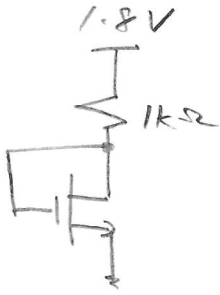
9. Find $\frac{W}{L}$. $I_D = 1 \text{ mA}$, $\mu C_{ox} = 200 \mu\text{A/V}^2$, $V_{th} = 0.5 \text{ V}$



$$V_{GS} = 1.8 \text{ V} - 1 \text{ mA} \times 1 \text{ k}\Omega = 0.8 \text{ V}$$

$$\frac{W}{L} = \frac{I_D}{\frac{1}{2} \mu C_{ox} (V_{GS} - V_{th})^2} = \frac{1 \text{ m}}{\frac{1}{2} 200 \mu (0.8 - 0.5)^2} = 111$$

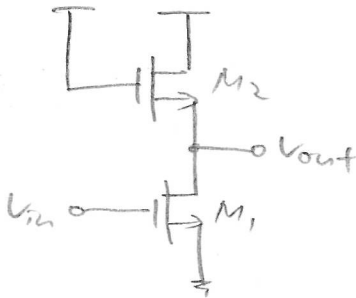
10. Find gain. $(\frac{W}{L})_1 = 100$, $(\frac{W}{L})_2 = 1$, $\lambda = 0$.




$$\frac{V_{out}}{V_{in}} = -g_{m1} \times \frac{1}{g_{m2}} = -\frac{\sqrt{2 \mu C_{ox} (\frac{W}{L})_1 I_D}}{\sqrt{2 \mu C_{ox} (\frac{W}{L})_2 I_D}} = -\sqrt{\frac{(\frac{W}{L})_1}{(\frac{W}{L})_2}} = -10$$

$$g_m = \sqrt{2 \mu C_{ox} \frac{W}{L} I_D}$$

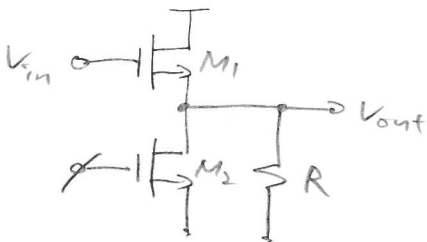11. Find gain. $\lambda_1 = 0$, $\lambda_2 \neq 0$.




S.S.

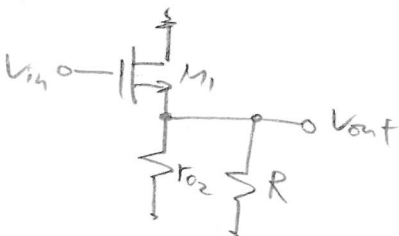


From table :

$$\frac{V_{out}}{V_{in}} = \frac{-g_{m1} (r_{o2} \parallel R)}{1 + g_{m1} (r_{o2} \parallel R)}$$

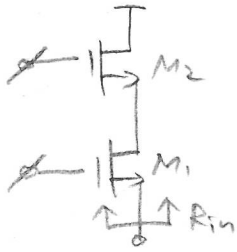
12. Find R_{in} . $\lambda_1 \neq 0$, $\lambda_2 = 0$.



S.S.

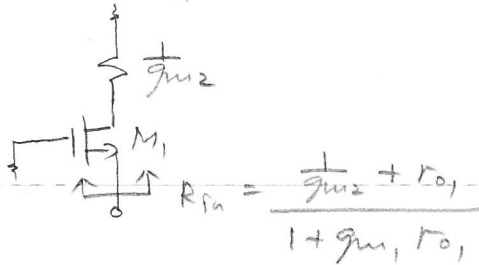

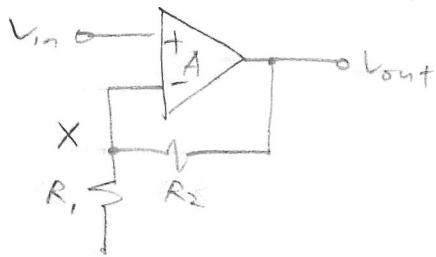13. Find gain. $A = 1000$, $R_1 = 1k\Omega$, $R_2 = 9k\Omega$.




$$V_x = V_{out} \frac{R_1}{R_1 + R_2}$$

$$V_{out} = A (V_{in} - V_x) = A \left(V_{in} - V_{out} \frac{R_1}{R_1 + R_2} \right)$$

$$V_{out} \left(1 + A \frac{R_1}{R_1 + R_2} \right) = A V_{in}$$

$$\frac{V_{out}}{V_{in}} = \frac{A}{1 + A \frac{R_1}{R_1 + R_2}} = \frac{1000}{1 + 1000 \frac{1k}{1k + 9k}} = 9.9$$

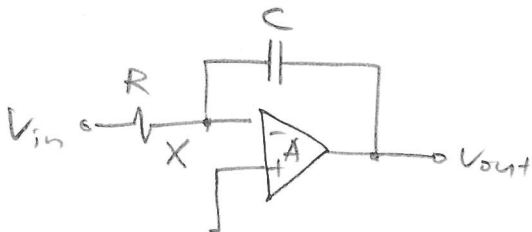14. Find V_{out} . $V_{in} = V_0 \sin(t)$, $A = \infty$.



Because $A = \infty$, $V_x = 0V$.


KCL @ X

$$\frac{V_{in}}{R} + C \frac{dV_{out}}{dt} = 0$$

$$dV_{out} = -\frac{V_{in}}{RC} dt$$

$$V_{out} = \frac{-1}{RC} \int V_{in} dt = \frac{1}{RC} \cos(t)$$

15. Find gain, $\lambda \neq 0$.


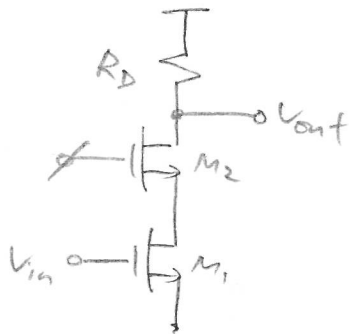


$$\frac{V_{out}}{V_{in}} = -G_m R_{out} = -g_{m1} (R_D \parallel g_{m2} r_{o2} r_{o1})$$

$$G_m \approx g_{m1}$$

$$R_{out} \approx R_D \parallel g_{m2} r_{o2} r_{o1}$$

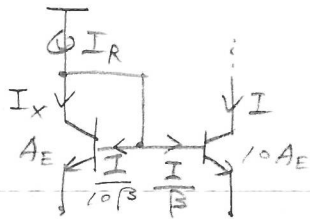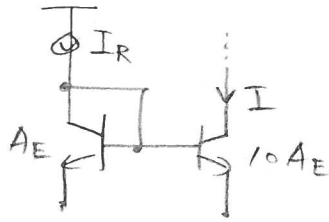16. Find I . $I_R = 1 \text{ mA}$, $\beta = 100$.



$$I = 10 I_X$$


$$I_X = I_R - \frac{I}{10\beta} - \frac{I}{\beta}$$

$$I = 10 I_R - \frac{I}{\beta} - 10 \frac{I}{\beta}$$

$$I \left(1 + \frac{10}{\beta} \right) = 10 I_R$$

$$I = \frac{10}{1 + \frac{10}{\beta}} I_R = 9.09 \text{ mA}$$

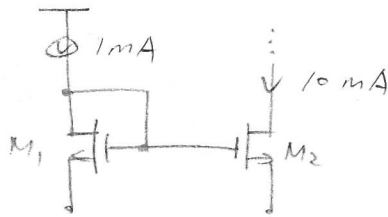17. Find L_2 . $\left(\frac{W}{L} \right)_1 = 10$, $W_2 = 20 \mu\text{m}$




$$\frac{\left(\frac{W}{L} \right)_2}{\left(\frac{W}{L} \right)_1} = \frac{10 \text{ mA}}{1 \text{ mA}}$$


$$\frac{W_2}{\left(\frac{W}{L} \right)_1} \times \frac{1 \text{ mA}}{10 \text{ mA}} = L_2 = 0.2 \mu\text{m}$$

5.

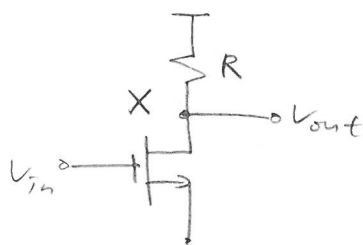18. Find ω_{Px} . $R = 1k\Omega$, $r_o = 20k\Omega$, $C_{GS} = 10fF$, $C_{GD} = 0fF$, $C_{SB} = C_{DB} = 2fF$.




S.S., ground i/p.

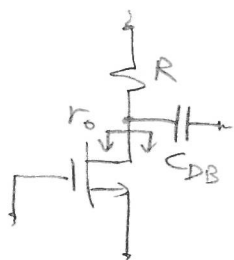


$$\omega_{Px} = \frac{1}{(R \parallel r_o) C_{DB}} = 5.25 \times 10^{11} \text{ rad/s}$$

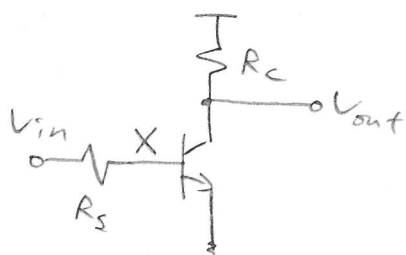19. Find ω_{Px} using Miller's theorem. $g_m = 1mS$, $r_o = 20k\Omega$, $r_\pi = 100k\Omega$, $R_S = 50\Omega$, $R_C = 10k\Omega$, $C_\pi = 10fF$, $C_\mu = 20fF$, $C_{CS} = 40fF$.



S.S., Miller's, ground i/p.

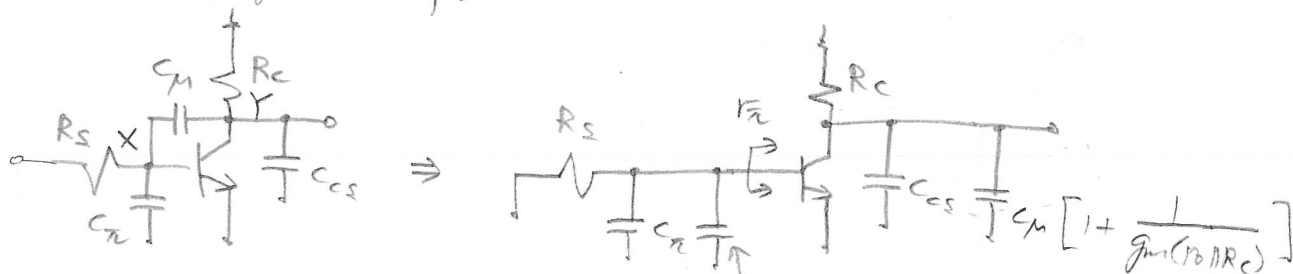


$$\text{gain } X \text{ to } Y = -g_m(r_o \parallel R_C) = -6.667 \quad C_\mu [1 + g_m(r_o \parallel R_C)]$$

$$\omega_{Px} = \frac{1}{(R_S \parallel r_\pi) \{ C_\pi + C_\mu [1 + g_m(r_o \parallel R_C)] \}}$$


$$= \frac{1}{49.98\Omega \times 1.633 \times 10^{-13} F}$$

$$= 1.23 \times 10^{11} \text{ rad/s}$$

20. Find C_{in} .


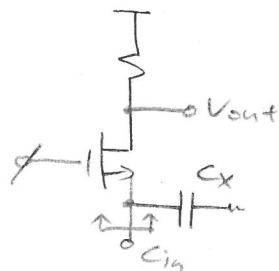


S.S., ground i/p.

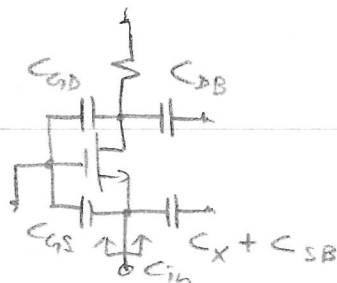


$$C_{in} = C_{gs} + C_x + C_{sb}$$

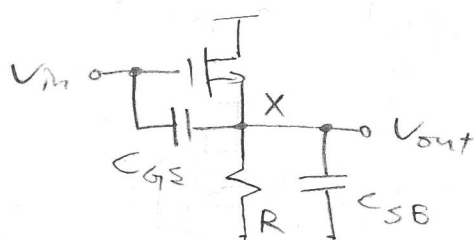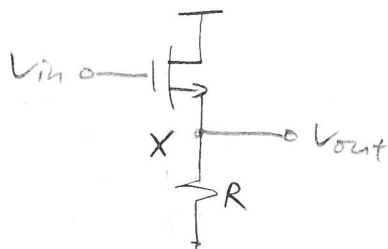21. Find ω_{Px} . Use Miller's. $\lambda \neq 0$.




gain from V_{in} to X is $\frac{g_m r_o R}{R + r_o + g_m r_o R} = A$ (from CD in table)

S.S., Miller's, ground i/p.

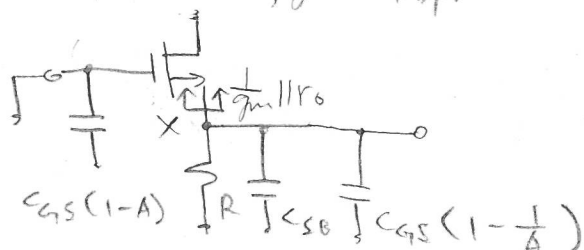


$$\omega_{Px} = \frac{1}{\left(\frac{1}{g_m} \parallel r_o \parallel R \right) \left[C_{sb} + C_{gs} \left(1 - \frac{1}{A} \right) \right]}$$

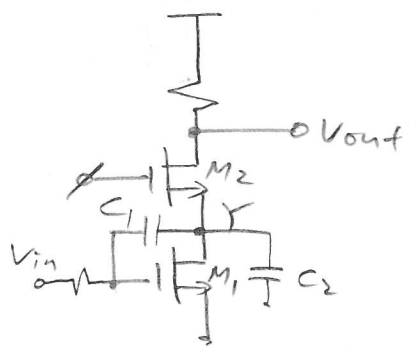22. Find the total cap. that Y sees to ground. Use Miller's.
Ignore all parasitic caps. $\lambda = 0$.




S.S.
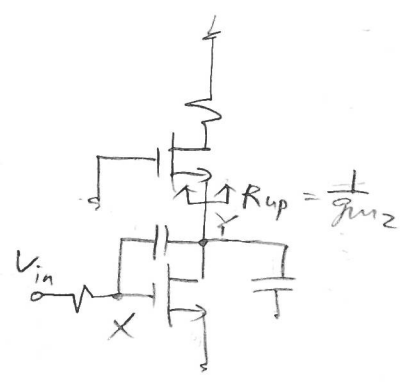
$$\text{gain } X \text{ to } Y = -g_{m1} \frac{1}{g_{m2}}$$



S.S., use Miller's, ground i/p.

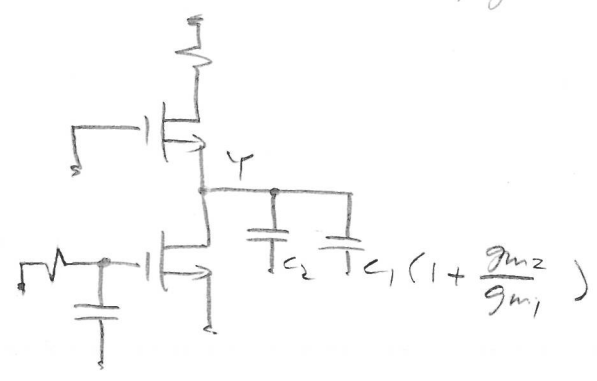

$$C_Y = C_2 + C_1 \left(1 + \frac{g_{m2}}{g_{m1}} \right)$$

