

10/7/15  
10/7/15

# ECEN 340 LAB 4 Notes

$$A = 5 = \frac{R_c}{\frac{V_{CE} - V_{CE(sat)}}{I_c} + R_E}$$

Re calculation

Choose  $R_E = 100 \Omega$

$$5 = \frac{R_c}{(20mV) \frac{R_c}{4.5V} + 100 \Omega}$$

$$0.02889 R_c + 500 \Omega = R_c$$

$$500 \Omega = 0.9711 R_c$$

$$R_c = 514.87 \Omega$$

$$V_{out, DC} = 4.5 = R_c I_c$$

Ic calculation

$$I_c = \frac{4.5}{R_c}$$

$$I_c = \frac{4.5V}{514.87 \Omega}$$

$$I_c = 8.74 \text{ mA}$$

R1, R2 calculation

See note on voltage divider

$$I_c = \frac{V_{CE}}{R_E} = \frac{V_B - V_{BE}}{R_E} = \frac{1}{R_E} \left( V_{CC} \frac{R_2}{R_1 + R_2} - V_{BE} \right) = I_c$$

$$V_{CC} \frac{R_2}{R_1 + R_2} \gg V_{BE} \therefore I_c \approx \frac{1}{R_E} V_{CC} \frac{R_2}{R_1 + R_2}$$

$$I_c = \frac{1}{R_E} V_{CC} \frac{R_2}{R_1 + R_2}$$

$$\frac{R_E I_c}{V_{CC}} = \frac{R_2}{R_1 + R_2}$$

$$\frac{R_2}{R_1 + R_2} = \frac{(100 \Omega)(8.74 \text{ mA})}{9V} = 0.09711$$

$$\frac{R_2}{R_1 + R_2} \approx 0.0971$$

$$R_2 = 0.097(R_1 + R_2)$$

$$R_2 \approx 0.097R_1 + 0.097R_2$$

$$0.90R_2 \approx 0.097R_1$$

$$9.29 R_2 \approx R_1$$

Impedance of BJT


$$\beta R_E + r_\pi$$

$$\beta R_E + r_\pi \approx 10,000 \Omega$$

If  $\beta R_E \gg R_2$ , then

$$R_2 \parallel R_{in} \approx R_2$$

$$\text{Let } R_2 \approx 100 \Omega$$

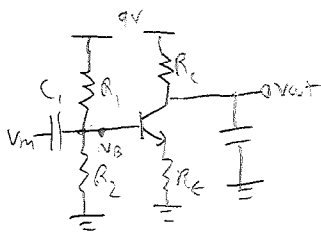

The voltage divider used in the derivation of  $I_c$  in terms of  $R_1, R_2, R_E$ , and  $V_{CE}$  should actually replace  $R_2$  with  $R_2 \parallel R_{in}$  (with  $R_{in}$  being the input resistance of the BJT as seen from  $V_B$ ). If we let  $R_{in} \gg R_2$ , then we can use the simplification  $R_2 \parallel R_{in} \approx R_2$

$$R_2 = 100 \Omega$$

$$R_1 = (100 \Omega)(9.29) = 929 \Omega$$

Actual resistor values that we have

$$R_2 = 100 \Omega$$

$$R_1 = 1 \text{ k}\Omega$$

Input impedance

$$R_{in} = (r_\pi + (\beta + 1)R_E) \parallel R_1 \parallel R_2$$

$$R_{in} = (r_\pi + (\beta + 1)(100 \Omega)) \parallel (1 \text{ k}\Omega) \parallel (200 \Omega)$$

$$(1 \text{ k}\Omega) \parallel (200 \Omega) = 90.91 \Omega$$

$$R_{in} = (r_\pi + (\beta + 1)(100 \Omega)) \parallel 90.91 \Omega$$

$$r_\pi + (\beta + 1)(100 \Omega) \approx \beta(100 \Omega) \gg 90.91 \Omega$$

$$\therefore \beta(100 \Omega) \parallel 90.91 \Omega \approx 90.91 \Omega$$

$$R_{in} = 90.91 \Omega$$

Output impedance

$$R_{out} \approx R_c$$

$$R_{out} = 514.87 \Omega$$

20.6V  
7.4V  
1.3V